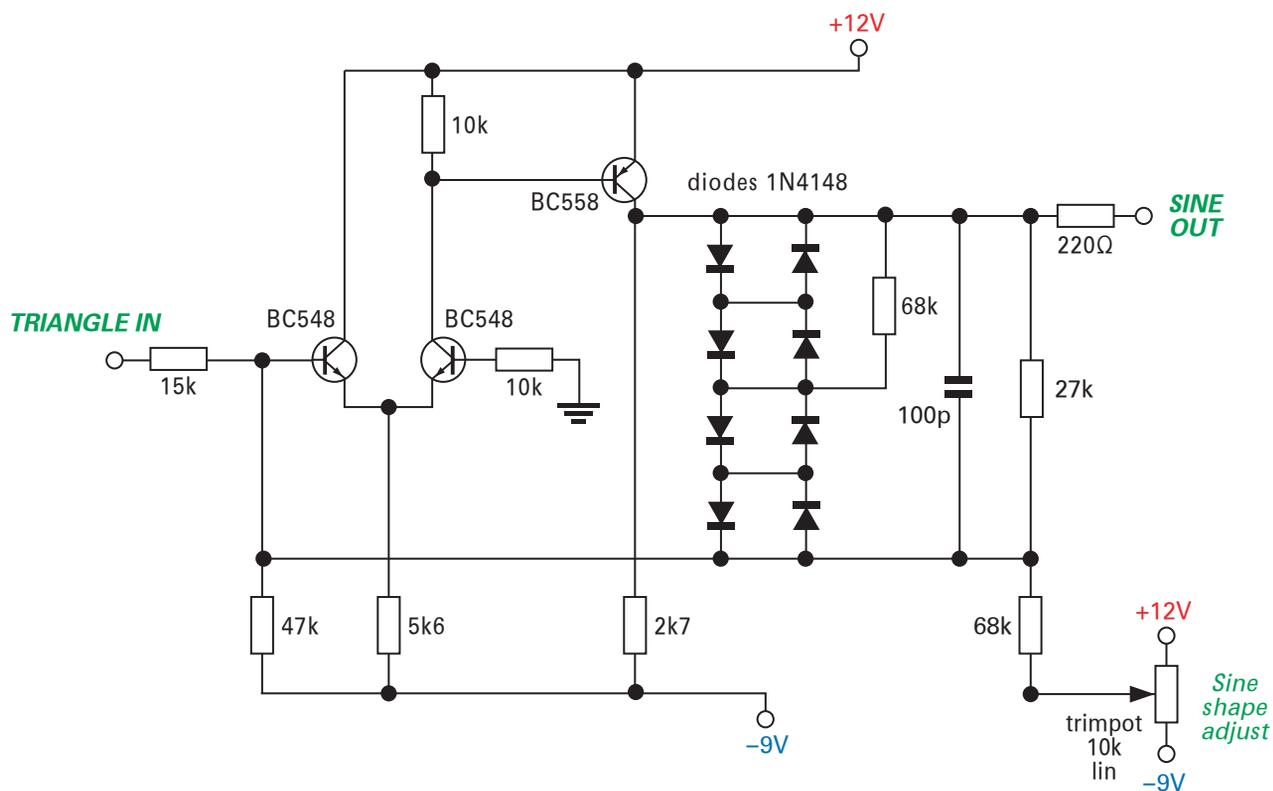


Triangle to Sine shaper



Lista de componentes

transistores

- 2 BC548
- 1 BC558

diodos

- 8 1N4148

resistores

- 1 220Ω – 1/8 W
- 1 2k7 – 1/8 W
- 1 5k6 – 1/8 W
- 2 10k – 1/8 W
- 1 15k – 1/8 W
- 1 27k – 1/8 W
- 1 47k – 1/8 W
- 2 68k – 1/8 W
- 1 10k – trimpot – 3362P

capacitor

- 1 100 pF – cerâmico

09/94
08/13
10/13